

CS 232 Lab 3 Q2

Arya Amin 200050014

1st February 2022

4-bit ripple carry adder(FourbitRipCarAdd.vhd)

I have designed the 4-bit ripple carry adder where 'a' and 'b' are the two 4-bit unsigned numbers that are to be added. 'cin' is a single-bit input carry that should be added with 'a' and 'b'. 'sum' is the 4-bit unsigned addition output and 'cout' is the single-bit output carry. It is designed only using the 1-bit full adder designed in the previous question.

The a 4-bit ripple carry adder Logical Expression is as follows,

$$\text{sum}(0) = \text{Full-Adder-Sum}(\text{a}(0), \text{b}(0), \text{cin}),$$
$$\text{sum}(1) = \text{Full-Adder-Sum}(\text{a}(1), \text{b}(1), \text{c0}),$$
$$\text{sum}(2) = \text{Full-Adder-Sum}(\text{a}(2), \text{b}(2), \text{c1}),$$
$$\text{sum}(3) = \text{Full-Adder-Sum}(\text{a}(3), \text{b}(3), \text{c2}),$$
$$\text{c0} = \text{Full-Adder-cout}(\text{a}(0), \text{b}(0), \text{cin}),$$
$$\text{c1} = \text{Full-Adder-cout}(\text{a}(1), \text{b}(1), \text{c0}),$$
$$\text{c2} = \text{Full-Adder-cout}(\text{a}(2), \text{b}(2), \text{c1}),$$
$$\text{cout} = \text{Full-Adder-cout}(\text{a}(3), \text{b}(3), \text{c2}),$$

Here c0, c1, c2 are single bit signals used to store carry at each addition.

Therefore using the above shown way I created the 4-bit ripple carry adder using only the 1-bit full adder where $A = a(i)$, $B = b(i)$ and $\text{cin} = \text{ci}$.

For each bit of addition we need one 1-bit Full Adder and therefore, total FullAdders required to design the 4-bit ripple carry adder is,

Full-Adders = 4